



CE Amplifier with current gain 10
designed by Amit Barman